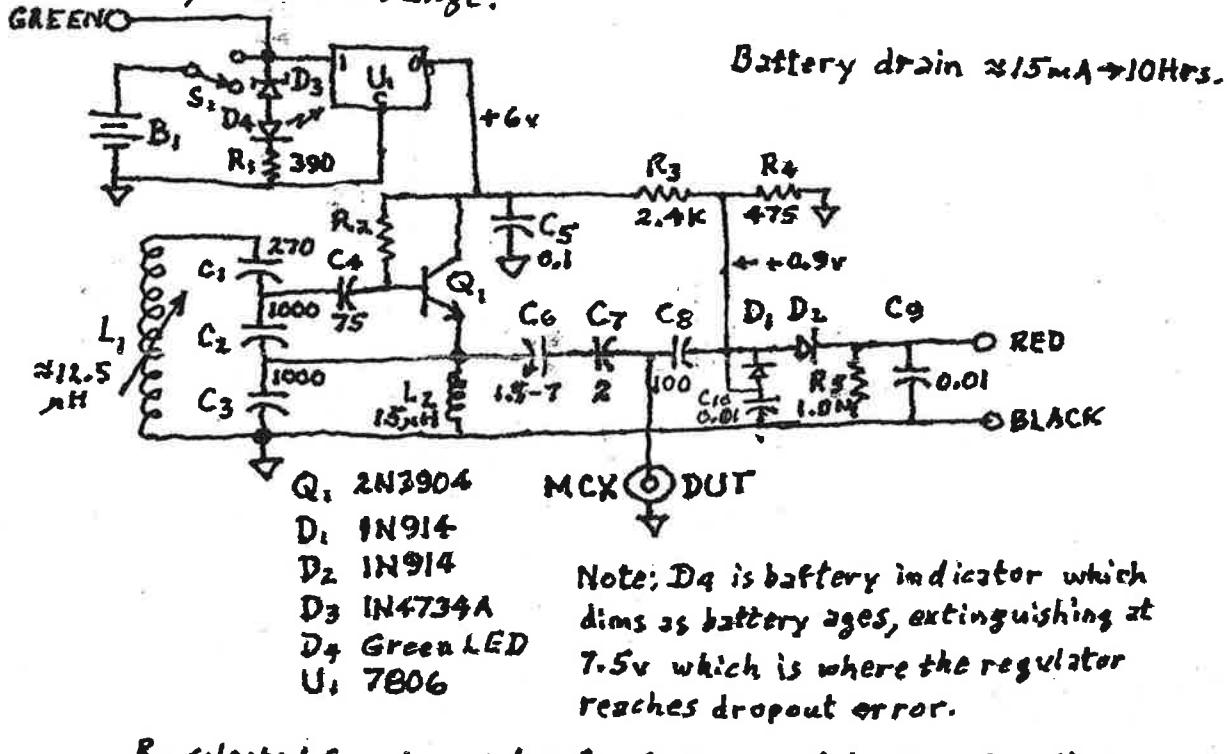


POSITION-SENSOR TESTER

The sensor is a tape-wound inductor with an inductance of about $15\mu H$ and has a 270 pF coaxial cable attached. The Q of this resonator is approximately 31, at a frequency of about 3.35 MHz . (In use, a lower frequency is used in a bridge circuit).

An oscillator, tunable in the vicinity of 3.35 MHz , having a fixed amplitude (regulated by power supply) is loosely coupled to the device under test (which plugs into a MCX coaxial connector) having a rectifier and voltmeter attached. A digital voltmeter is to be connected to the red and black terminals (marked V_o). The oscillator frequency is then adjusted for a maximum reading. The Q of the resonating sensor under test is about 10 times the DC voltage at V_o.

The tester is designed around a single sensor known to be good, but the frequency and Q of all sensors should fall in a very narrow range.



R₂ selected for transistor Q₁, 100K in unit 1, 200K in unit 2.