

# *EOM modification for modulation at 118MHz*

Rich Abbott, Koji Arai  
Commissioning F2F  
Apr. 9, 2018  
LIGO-G1800724 1/5

**ALIGO EOM has 3 electrodes & 3 RF ports for 3 mod. freq**

- Port1: 9.1MHz (IFO  $f_1$ ), Port2: 24.1MHz (IMC), Port3: 45.5MHz (IFO  $f_2$ )

**How do we arrange the 4 RF frequencies?**


- Port2 for 118.3MHz (resonant)
- Port3 for 45.5MHz (resonant) and 24.1MHz (non-resonant)

**Requirements & Results: response of the new unit**


Port	Freq [MHz]	Required Mod		EOM response [mradpk/Vpk]	Required RF	
		Acq [rad]	Opr [rad]		Acq [dBm]	Opr [dBm]
#1	9.1	0.22	0.11	42	24.3	18.3
#2	118.3	---	0.01	12		8.5
#3	24.1	0.014	---	2.4	25.4	
#3	45.5	0.28	0.20	43	26.2	23.3
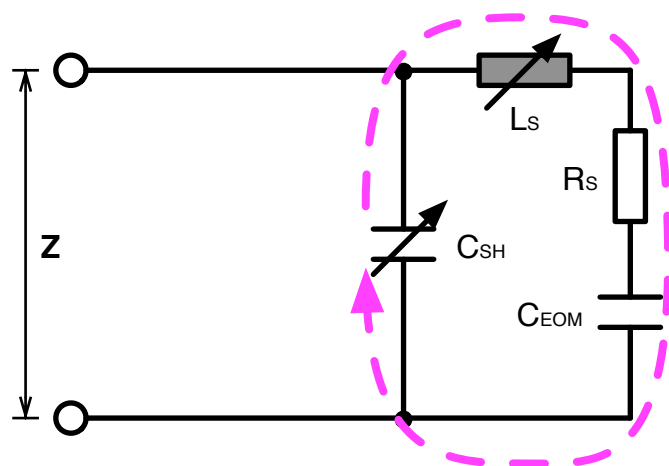
# EOM response

**Shunt C matching**  
(for 9.1MHz & 118.3MHz)







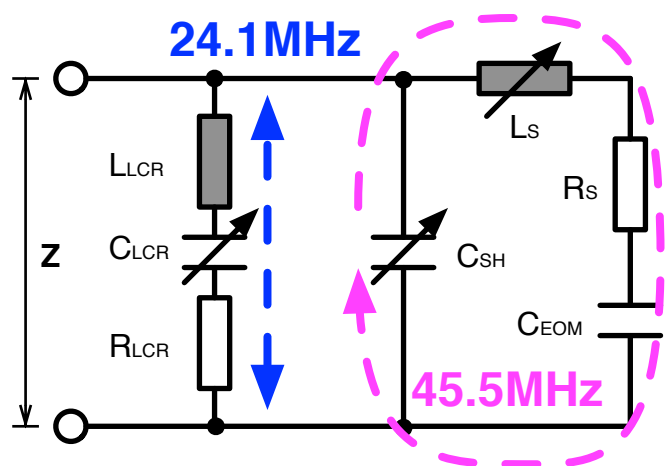**Shunt C+LCR matching**  
(for 45.5MHz+24.1MHz)



**Modulation Response [rad<sub>pk</sub>/V<sub>pk</sub>]**



Measured with a beat note of two lasers

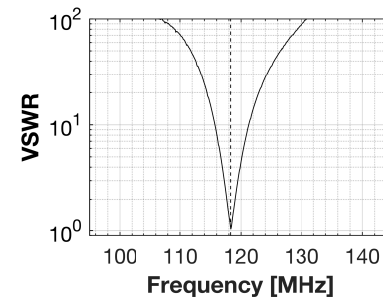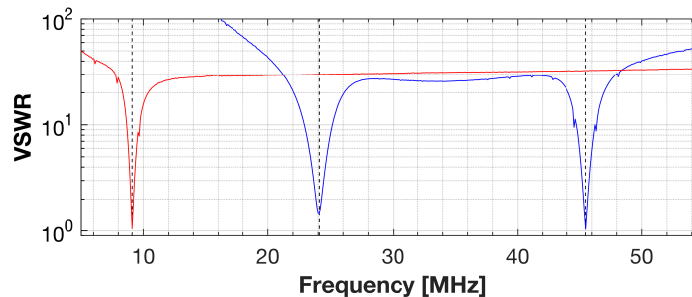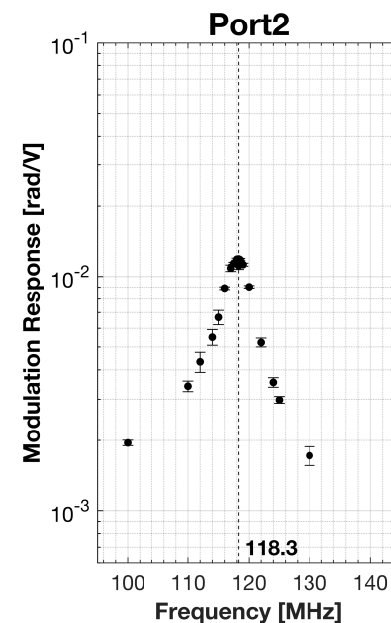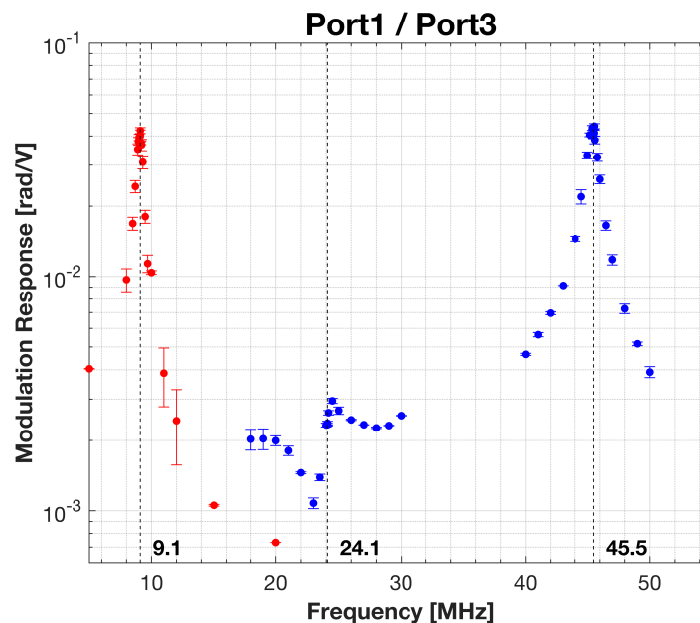
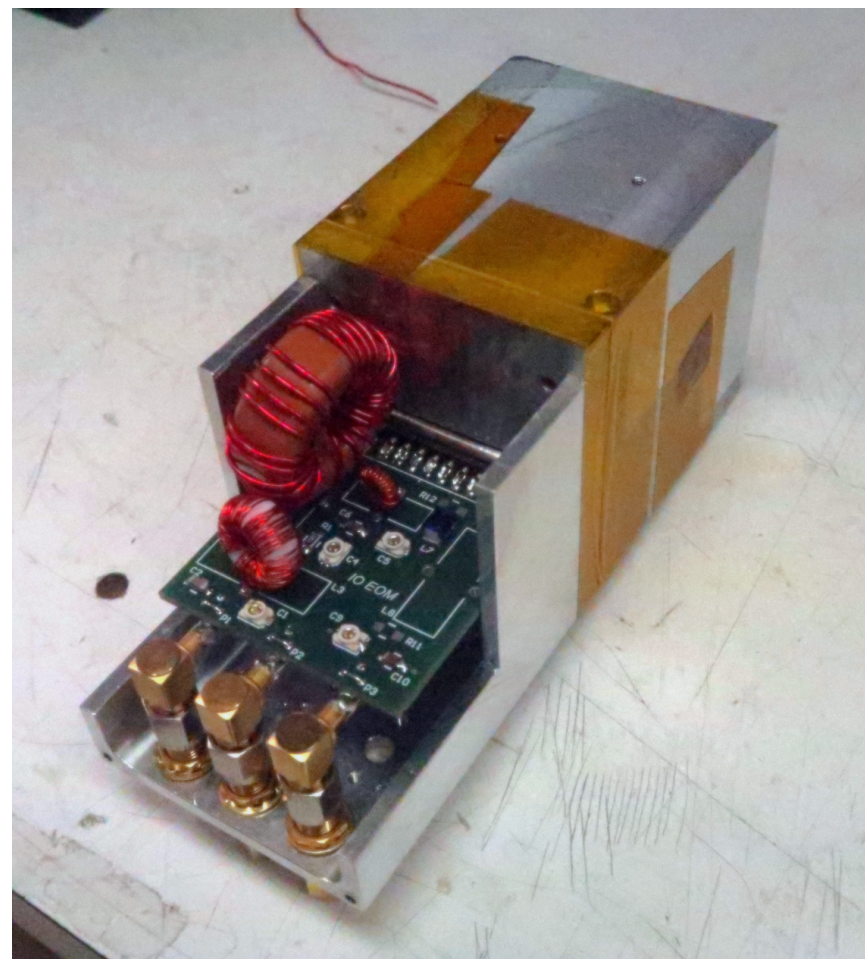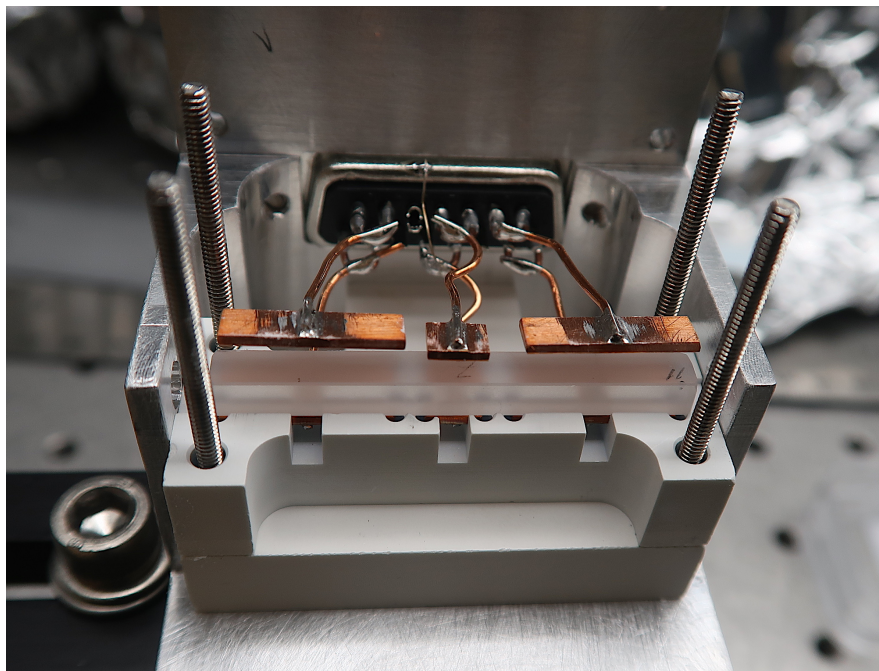
# EOM Crystal / Matching Circuit

LIGO-G1800724 3/5

RTP crystal: 4mm x 4mm x 40mm  
Plates: 14mm, 5mm, 14mm



Matching circuit  
Toroidal cores for 24/45/118MHz  
Chip L for 9MHz

# Installation remarks

- **The crystal was not tested with a high power beam**  
At least, the crystal needs FC cleaning
- **The crystal and the circuit are a matched pair.**  
The circuit will not work with the existing EOM crystal without serious tuning
- **Driving power**
  - 24.1MHz: 25dBm ~ requires an amplifier
  - 45.5MHz: 26dBm ~ still in the linear region of the AM stabilized driver
  - 9.1MHz: 24dBm ~ almost at the edge of the linear region
- **Use a power combiner for 45.5MHz & 24.1MHz**
- **Demod. phases and some of the LSC input matrix will change**  
cf. 27MHz comes from CRxSB3, SB1xSB-2, SB1xSB4(=f2-f1), ...
- **Matching circuit has no rid**  
because of a large toroidal L & to eliminate stray C  
do not touch the inductors  
=> the resonant freqs and the matching conditions will change

## o Polarization: determined by the polarization of JAC

- The JAX prelim design: S-pol
- The crystal is wedged horizontally for P-pol

## o Same 4 modulation freqs

## o Thermal lensing

- The input light power will be adjusted on the PSL
- Power adjustment => different thermal lense in the EOM
- How large is the lens? Which crystal should we use (RTP? SLT?)

## o Other thermal effect

- Temperature dependence of the inductance  
(ceramic core ~125ppm, vacuum core ?)

## o Residual AM?

- Feedback control?



# Production remarks

## Make loss (R) as small as possible

- intrinsic loss of the RTP crystal? (dielectric loss?)
- inductor loss (DCR/skin effect)
- loss in the PCB (skin effect)


## Stray capacitance

- Stray shunt capacitance
- capacitance in inductors
- housing metal



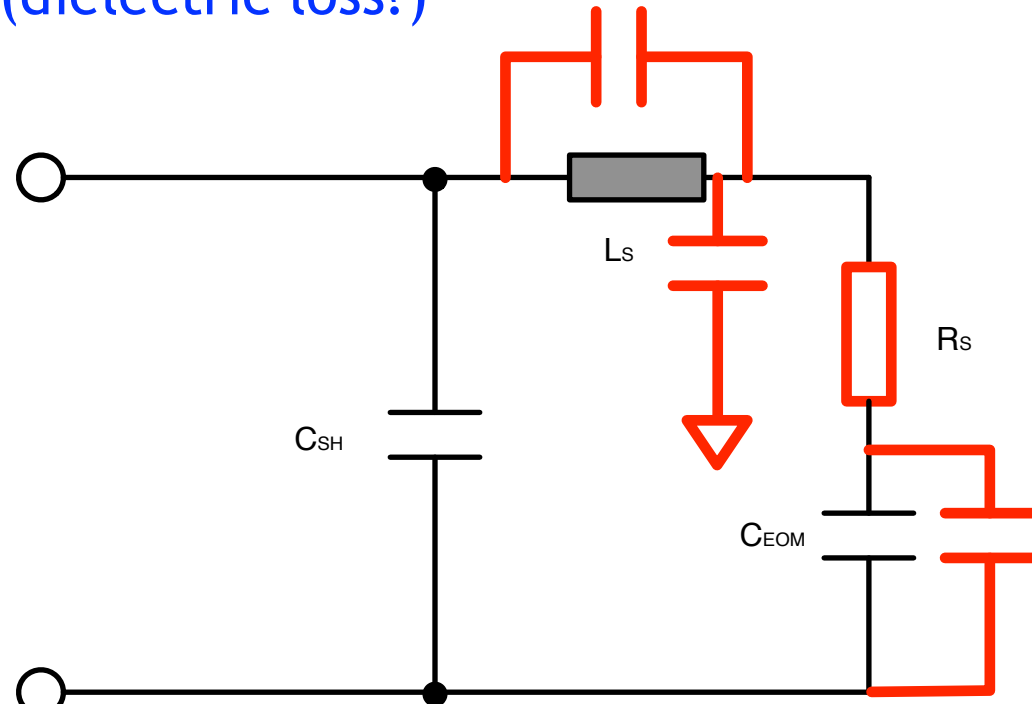
## Inductor stability

- distance from the housing metal
  - changes stray capacitance
- > changes the resonant freq
- > changes the modulation phase & amplitude

the housing has better shorting to ground






# Port1: 9.1MHz

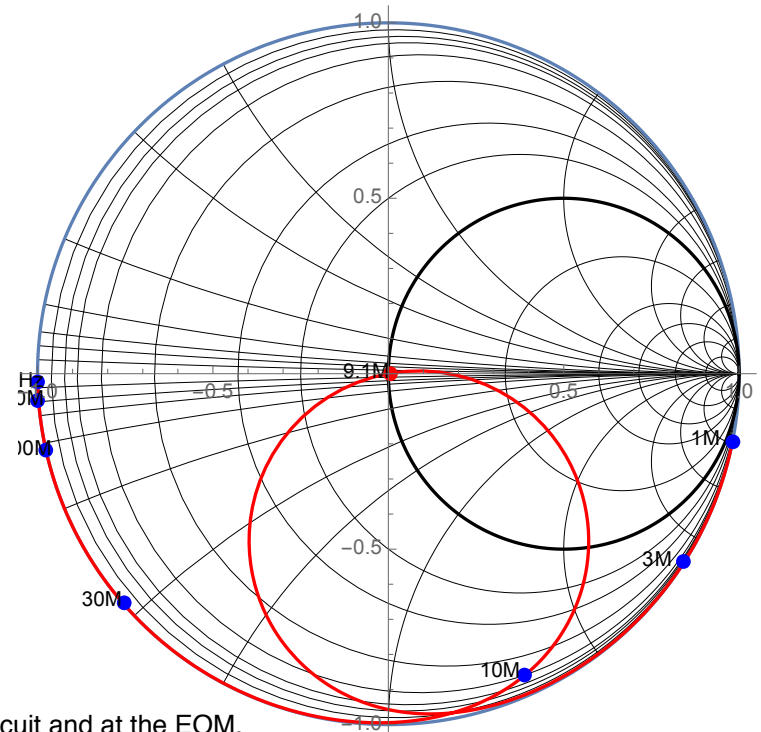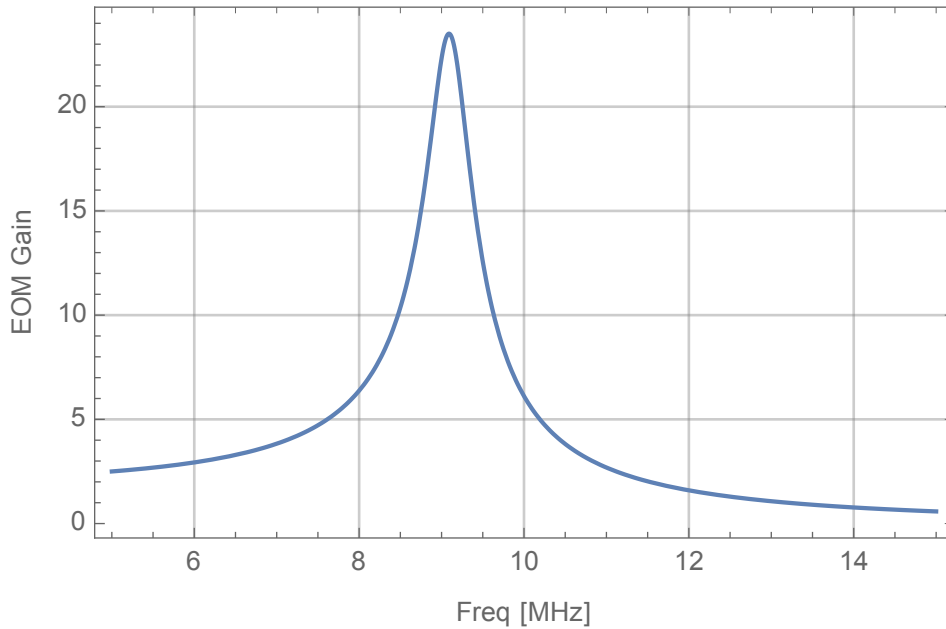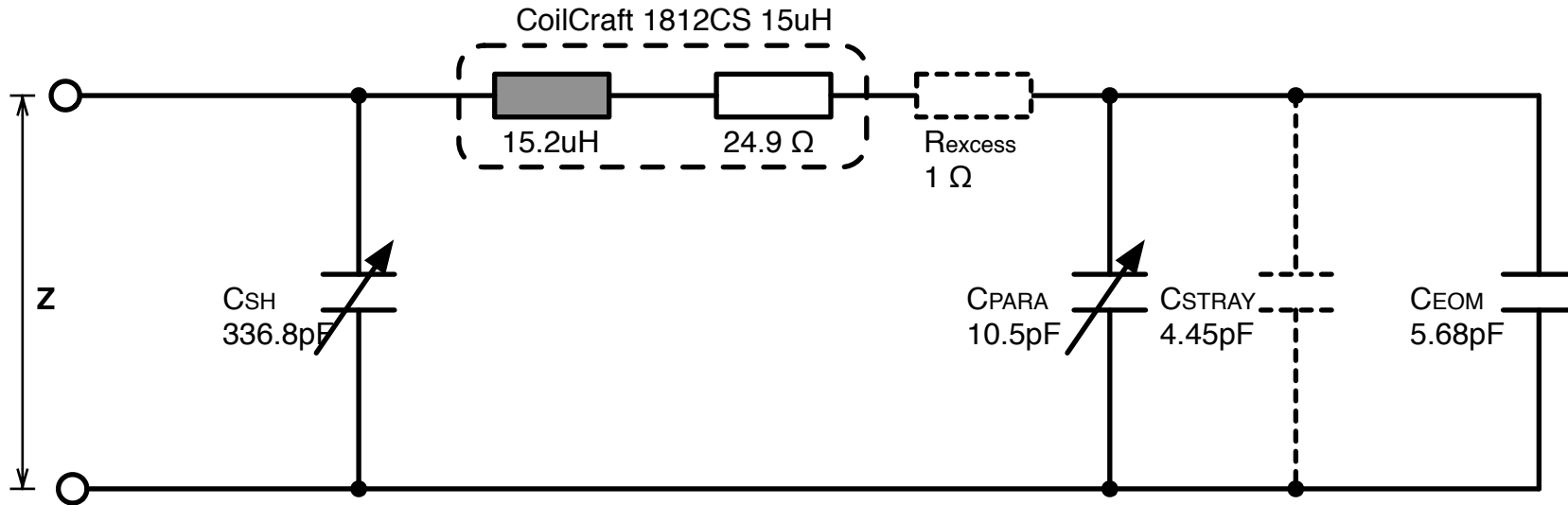

The EOM gain here is defined by the ratio of the voltages at the input of the matching circuit and at the EOM.






# Port2: 118.3MHz

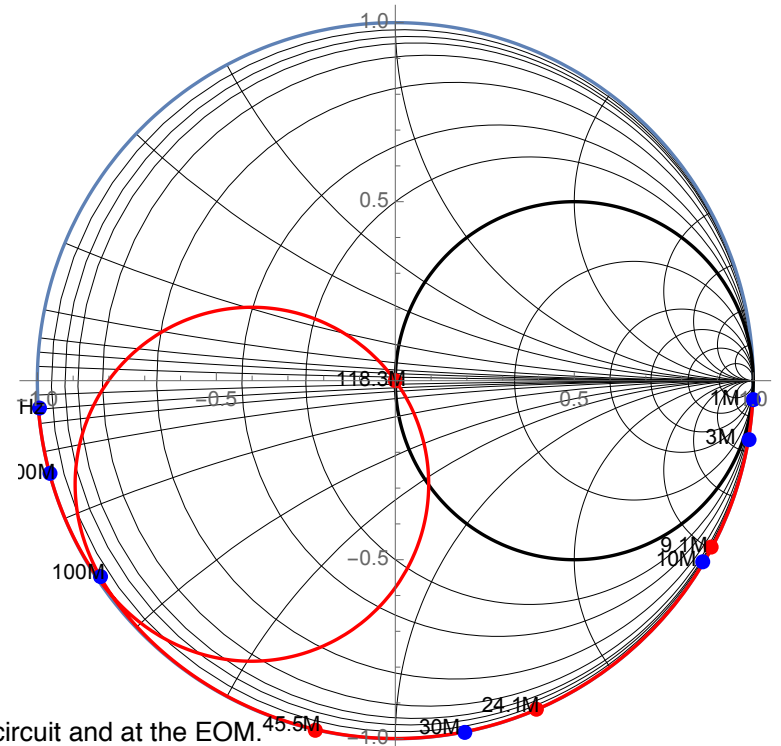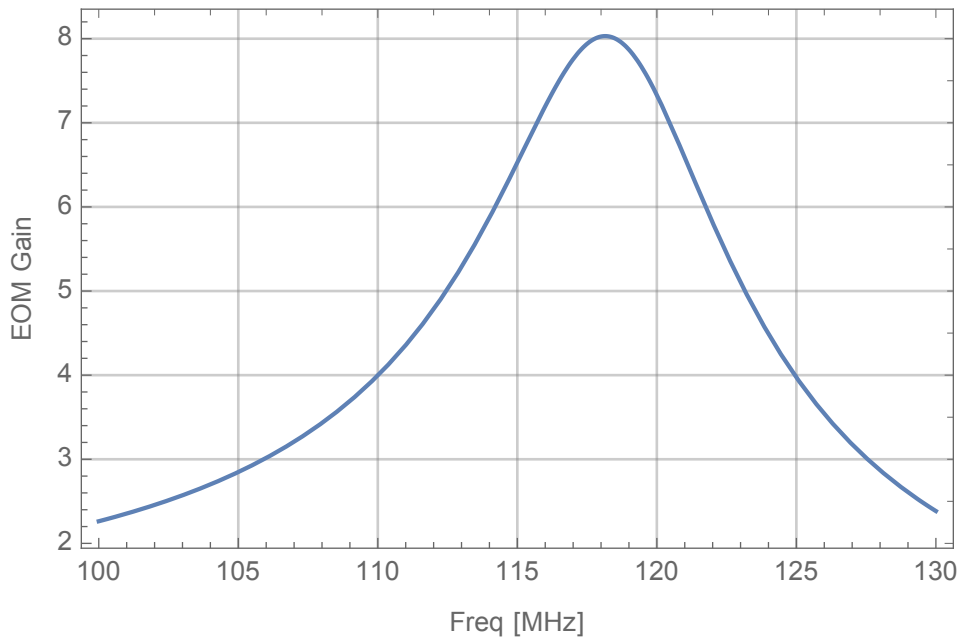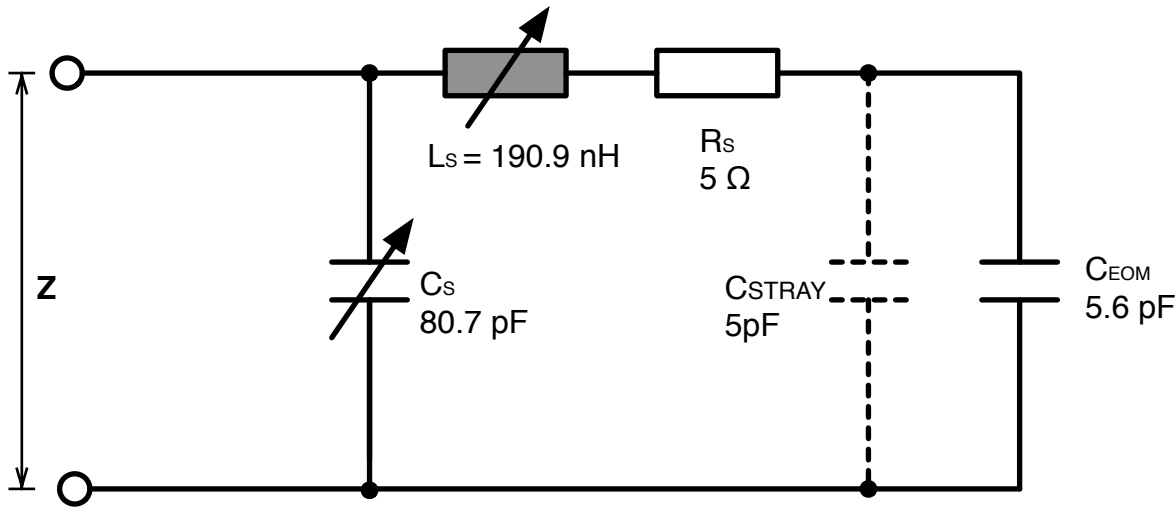

The EOM gain here is defined by the ratio of the voltages at the input of the matching circuit and at the EOM.

# Port3: 45.5MHz + 24.1MHz

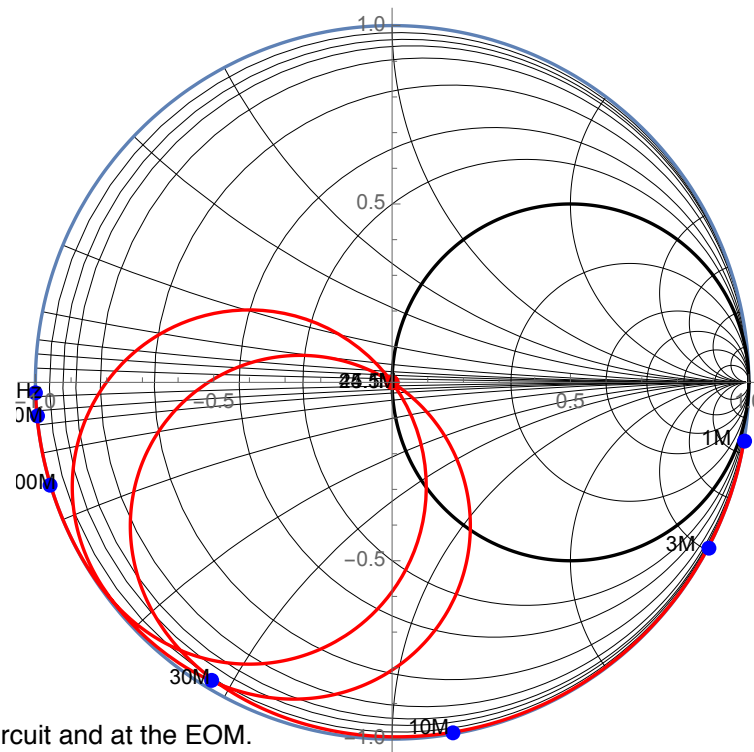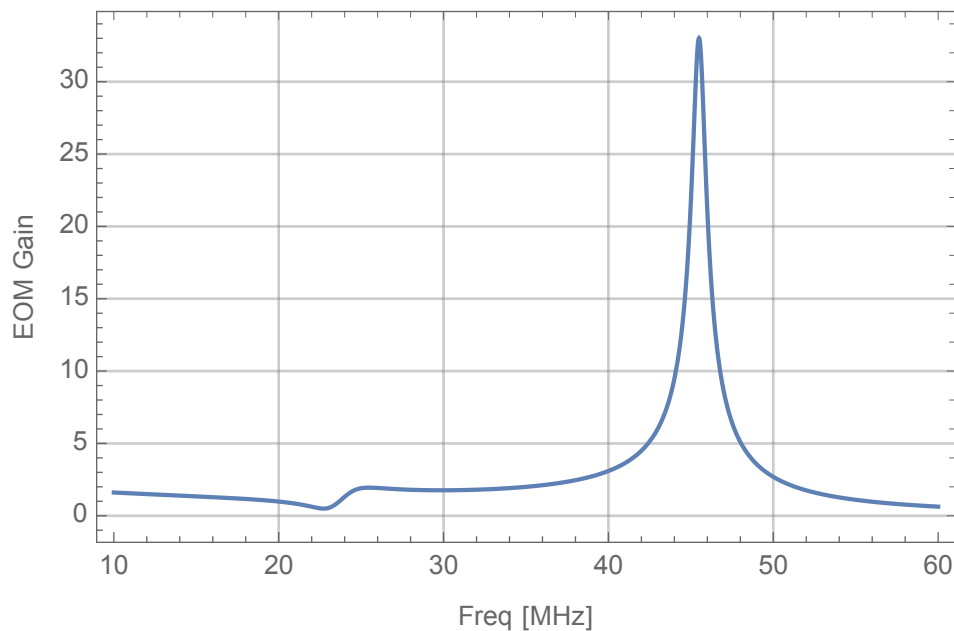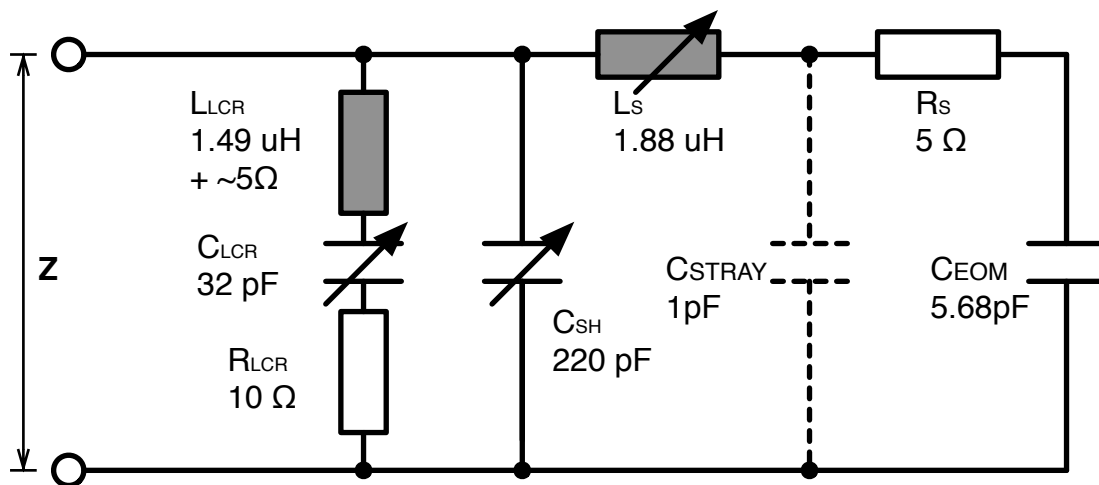

The EOM gain here is defined by the ratio of the voltages at the input of the matching circuit and at the EOM.

## EOM impedance measurement (March 29, 2018)

